
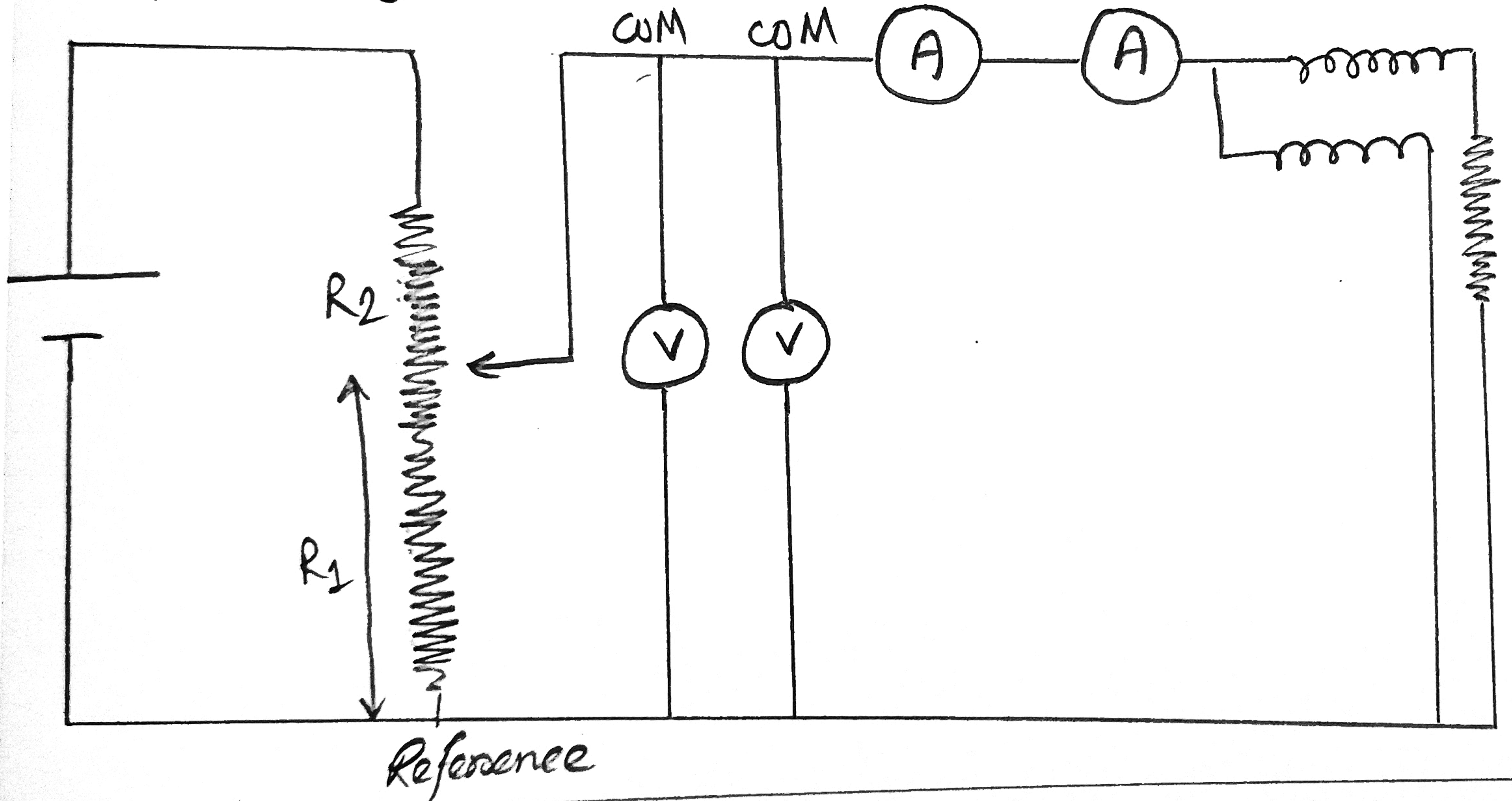



Circuit Diagram:

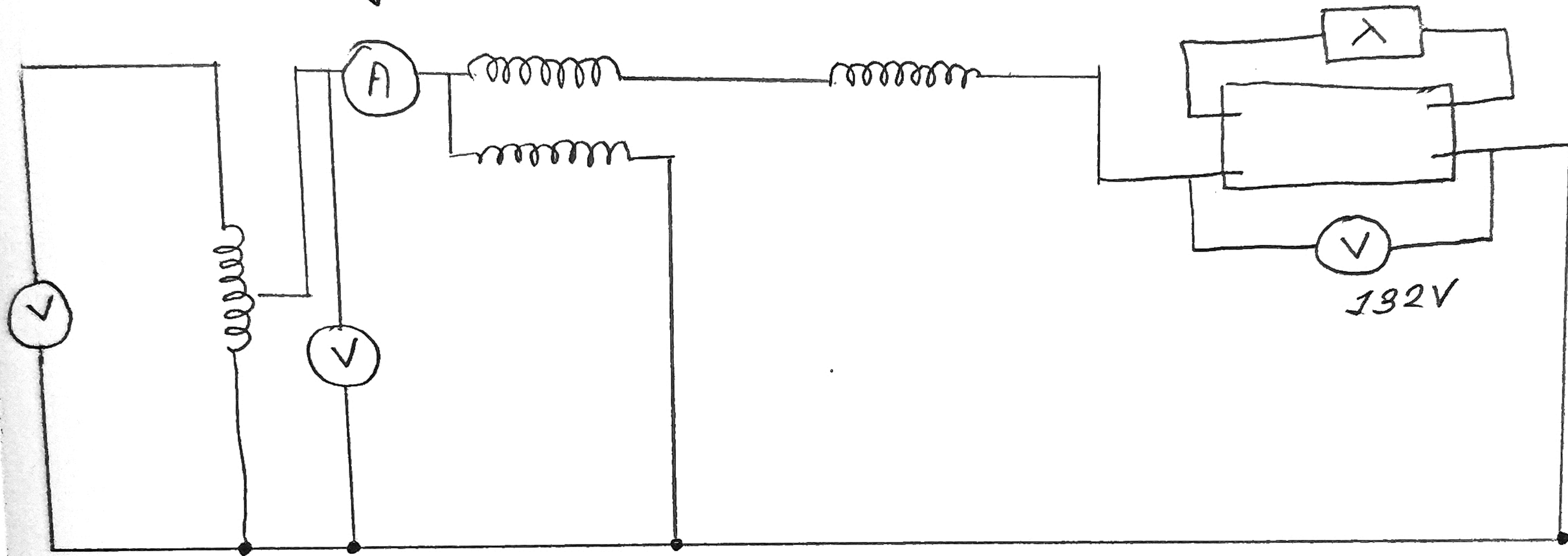


CALIBRATION OF AMMETER, VOLTMETER & WATTMETER

Circuit Diagram:




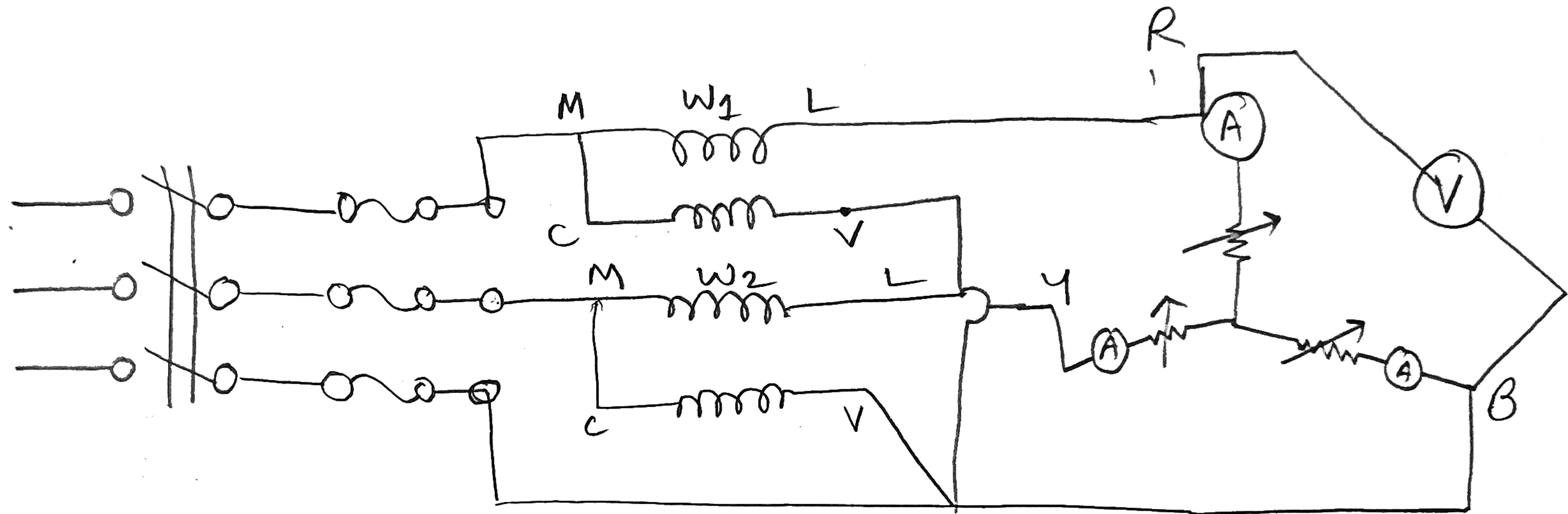

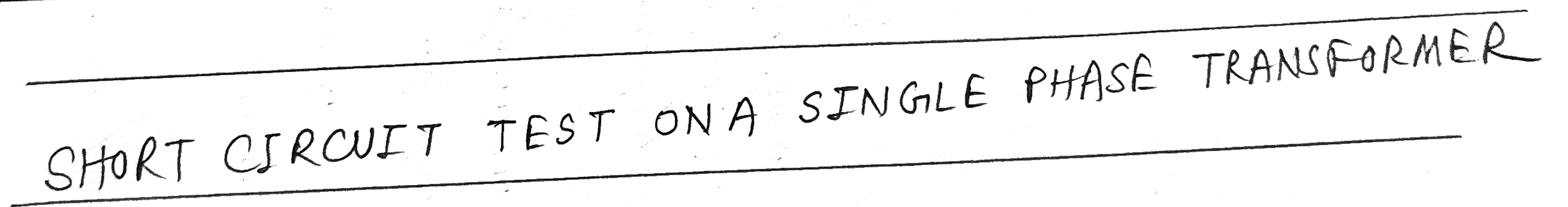Two wattmeters method of Measuring power in three phase circuit for resistance only




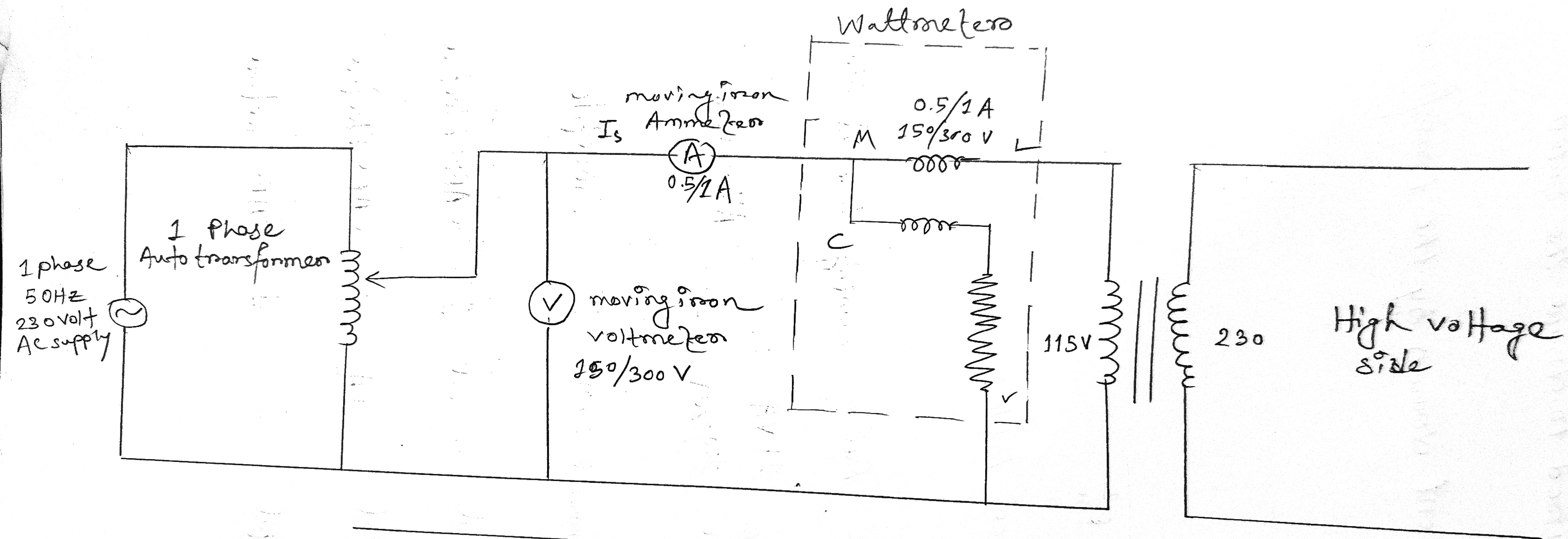SHORT CIRCUIT TEST ON A SINGLE PHASE TRANSFORMER



OPEN CIRCUIT TEST ON A SINGLE PHASE TRANSFORMER

Circuit Diagram:

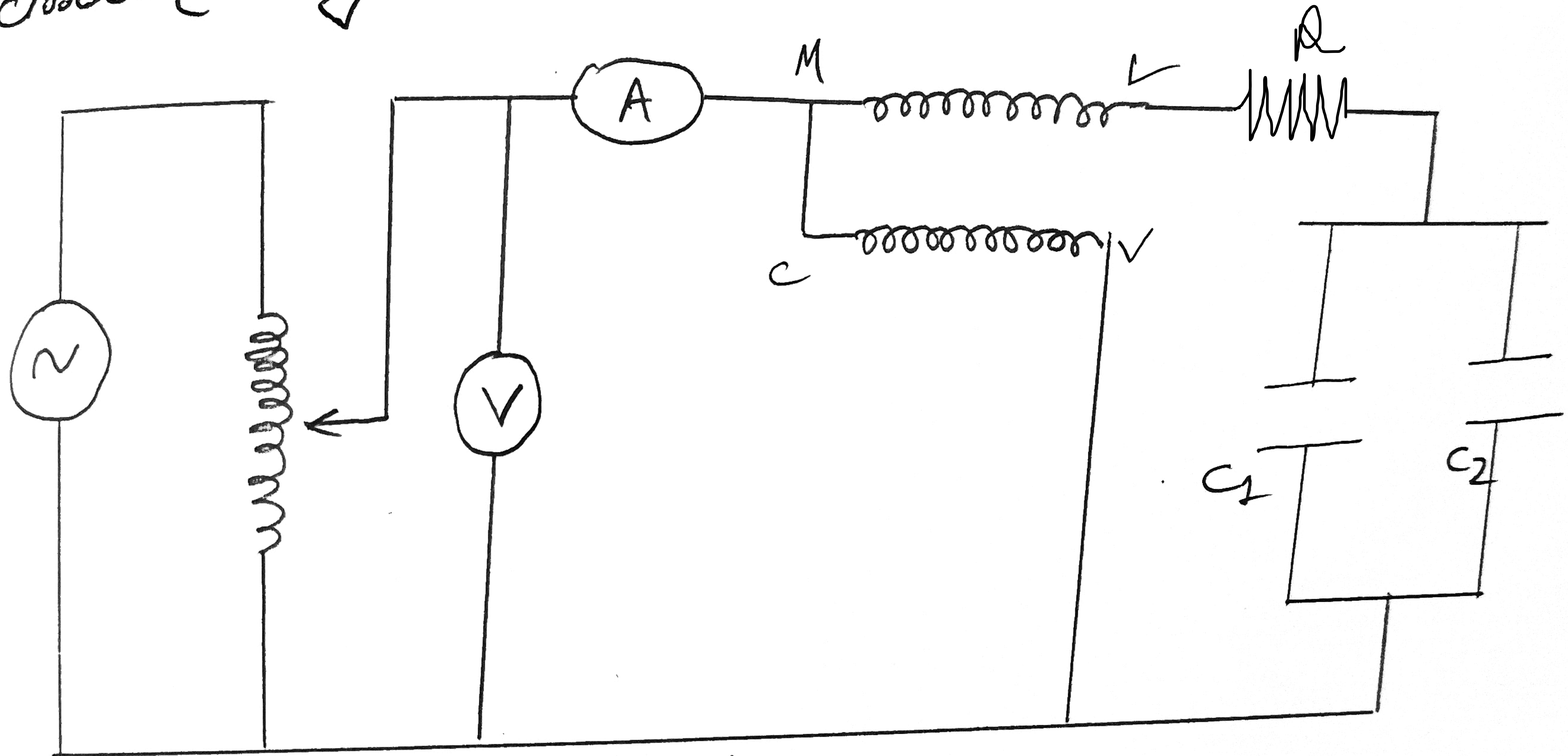

R-C SERIES CIRCUIT